

Discussion 8C


Circuits Review

- Transistors
- 1st order diff eq (RC)
- 2nd order diff eq (RLC)
- phasors
- filters
- resonance

- Problem

- Circuits Review WS Q7
- Sp20 MT1 Q6



I. Transistor Models

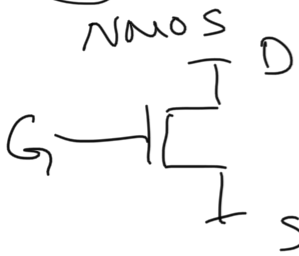

$$I_{DS} > 0$$

$$V_{tn} > 0$$


$$V_{GS} \geq V_{tn} \text{ to close}$$

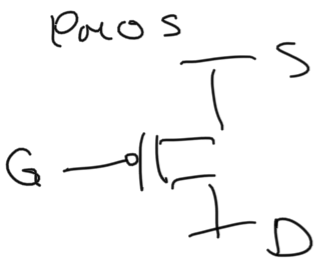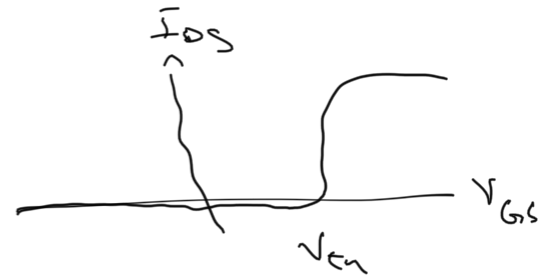

$$I_{DS} < 0$$


$$V_{tn} < 0$$

$$|V_{GS}| \geq |V_{ep}|$$

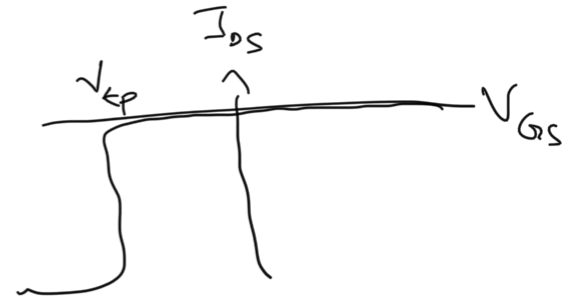

- Switch Model

(Digital logic gates)

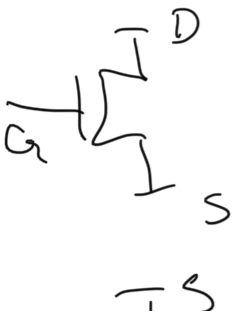


$$V_{GS} \geq V_{tn}$$


NMOS



• Resistor Switch Model
(power)

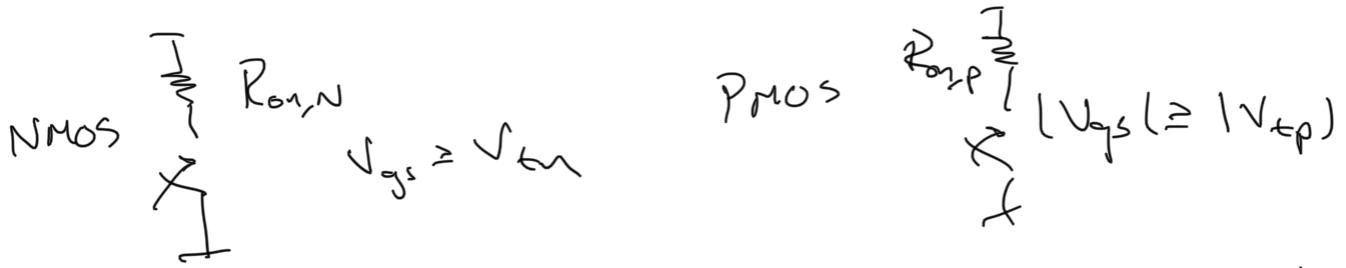

• RC Switch Model ← most important

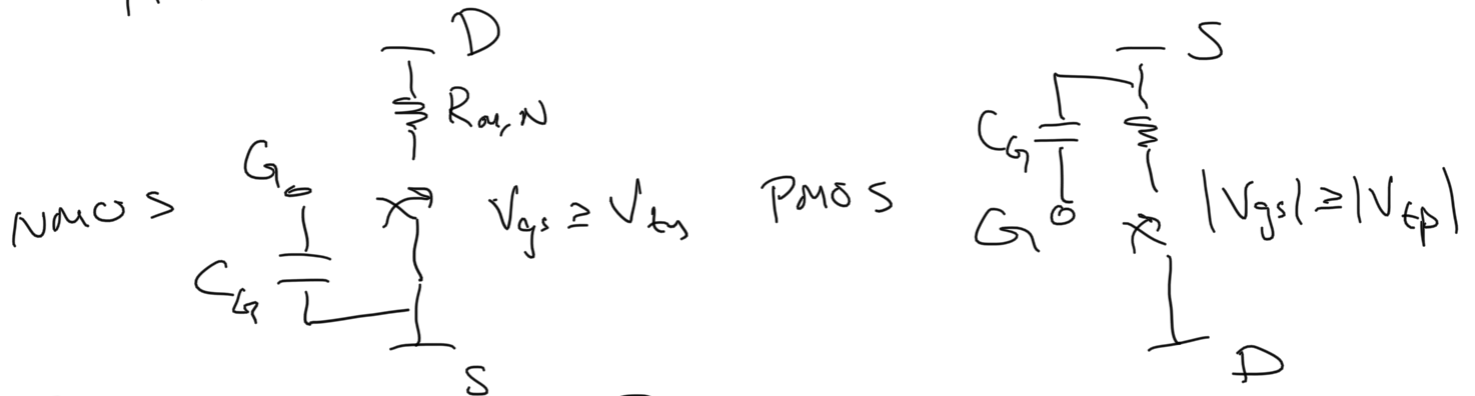

II. 1st Order D.F. Eqns

$$\frac{dx(t)}{dt} = \lambda x(t) + u(t)$$

• Homogeneous ($u(t) = 0$)


$$\frac{dx(t)}{dt} = \lambda x(t)$$

With initial condition $x(0) = x_0$

$$\Rightarrow \boxed{x(t) = x_0 e^{\lambda t}}$$

In ckt context, probably can guess something

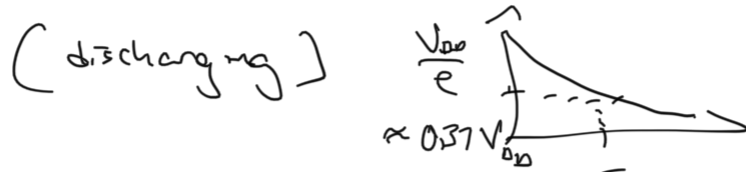like $V_{00} e^{-t/\tau}$ ← $\tau = RC$ (for RC ckt)




• Constant Input ($u(t) = b$)

$$\frac{dx(t)}{dt} = \lambda x(t) + b$$

$$x(t) = -\frac{b}{\lambda} + \left(x_0 + \frac{b}{\lambda}\right) e^{\lambda t}$$

w/ I.C. $x(0) = x_0$

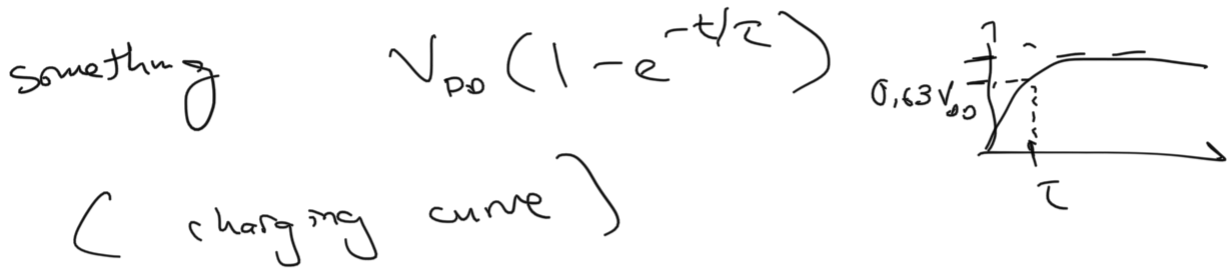In the context of ckt's, probably can guess something



• General case

$$\frac{dx(t)}{dt} = \lambda x(t) + u(t), \quad x(t_0) = x_0$$

$$x(t) = e^{\lambda(t-t_0)} x_0 + \int_{t_0}^t e^{\lambda(t-t')} u(t') dt'$$

(II) 2nd Order Diff Eq

Turn into matrix diff eq!

EX: series RLC, use V_c and $\frac{dV_c}{dt}$ as your state variables

Matrix diff. eq:

$$\frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = A \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

2nd order diff eq

$$\frac{d}{dt} \begin{bmatrix} V_c \\ \frac{dV_c}{dt} \end{bmatrix} = A \begin{bmatrix} V_c \\ \frac{dV_c}{dt} \end{bmatrix}$$

• Solution

$$\frac{d\vec{x}}{dt} = \begin{bmatrix} A_{11} & A_{12} \\ A_{21} & A_{22} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

By diagonalization argument?

$$x_i(t) = \sum_k C_k e^{\lambda_k t}$$

Procedure

(1) Guess $\begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} = \begin{bmatrix} \alpha_1 e^{\lambda_1 t} + \alpha_2 e^{\lambda_2 t} \\ \beta_1 e^{\lambda_1 t} + \beta_2 e^{\lambda_2 t} \end{bmatrix}^c$

(2) Evaluate $\vec{x}(0)$ and $\frac{d\vec{x}}{dt}(0)$ to obtain 4 eqns in 4 unknowns
... $\begin{bmatrix} \alpha_1 + \alpha_2 \end{bmatrix}$ $\begin{bmatrix} x_1(0) \end{bmatrix}$ ——— known

$$\vec{x}(0) = \begin{bmatrix} \dots \\ \beta_1 + \beta_2 \end{bmatrix} = \begin{bmatrix} x_1(0) \\ x_2(0) \end{bmatrix} \quad (\text{initial conditions})$$

$$\frac{d\vec{x}(t)}{dt} = \begin{bmatrix} \alpha_1 x_1 + \alpha_2 x_2 \\ \beta_1 x_1 + \beta_2 x_2 \end{bmatrix} = \mathbf{A} \begin{bmatrix} x_1(0) \\ x_2(0) \end{bmatrix} \quad \text{known}$$


③ Solve!

④ Phasors

Note that a sinusoid can be written as follows:

$$V_0 \cos(\omega t + \varphi) = \text{Re} \left\{ \underbrace{V_0 e^{j\varphi}}_{\tilde{V}} e^{j\omega t} \right\} = \frac{\tilde{V} e^{j\omega t} + \tilde{V}^* e^{-j\omega t}}{2}$$

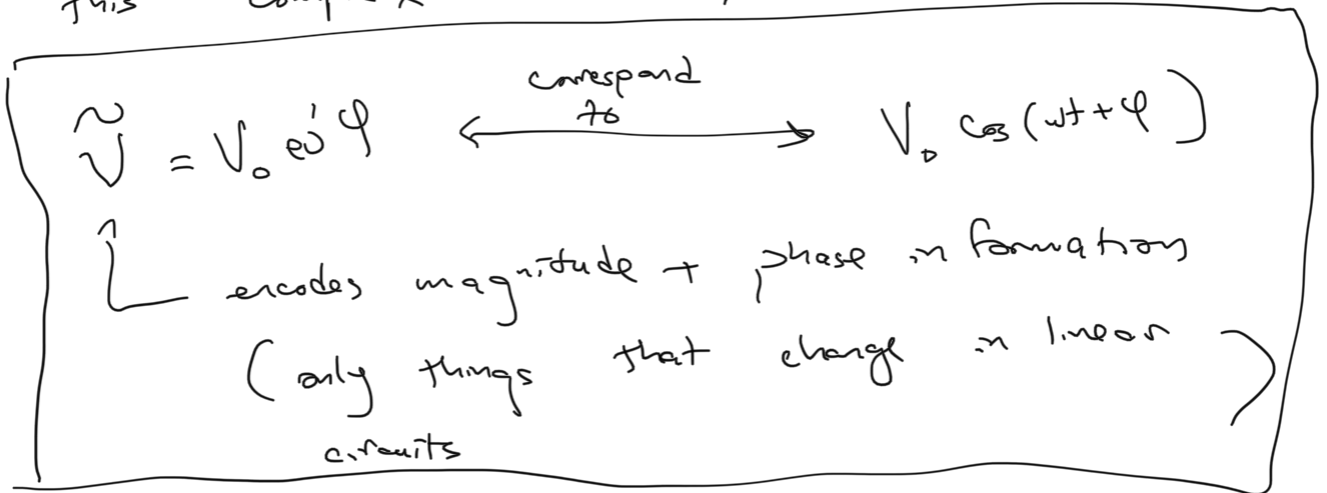Mathematically convenient to represent sinusoids as this complex number, the "phasor representation"



$$e^{j\omega t} \rightarrow \boxed{H} \rightarrow A e^{j\omega t}$$

↑ transfer function
...

Procedure

$H(j\omega)$

① Adopt a cosine reference

$$\sin(\omega t) = \cos(\omega t - \frac{\pi}{2})$$

② Transform circuit to phasor domain

$$R \rightarrow Z_R = R$$

$$L \rightarrow Z_L = j\omega L$$

$$C \rightarrow Z_C = \frac{1}{j\omega C}$$

③ Use KCL, KVL to solve!

④ Transform back to the time domain


$$V_{out} \cos(\omega t + \varphi) = \text{Re} \left\{ \tilde{V}_{out} e^{j\omega t} \right\}$$

$$\tilde{V}_{out} = V_{out} e^{j\varphi_{out}}$$

V. Filters


• Building Blocks

Simple RC LPIF

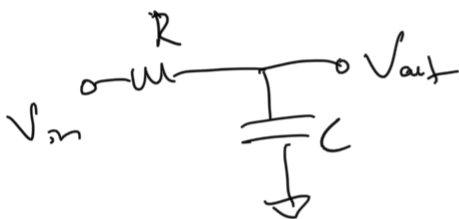



$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

Simple RC HPIF

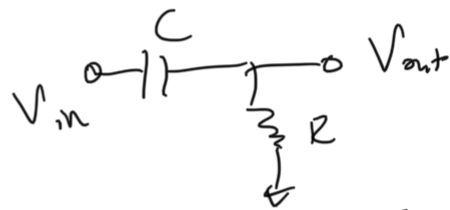

$$H(j\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

" Transfer functions have magnitude and phase
 $|H(j\omega)|$

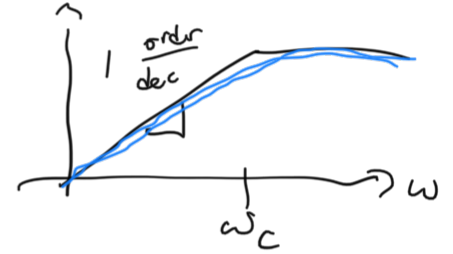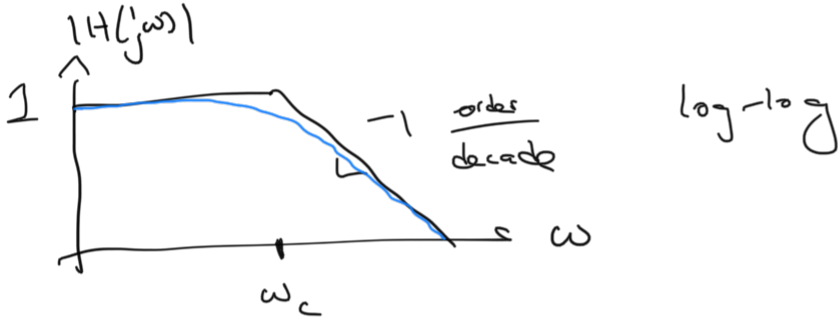



$\omega_c \equiv$ " corner / cutoff / 3dB / pole frequency "

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |H_{\max}|$$


LPF $H(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_c}}$

HPP $H(j\omega) = \frac{j\frac{\omega}{\omega_c}}{1 + j\frac{\omega}{\omega_c}}$

For simple RC, $\omega_c = \frac{1}{RC}$

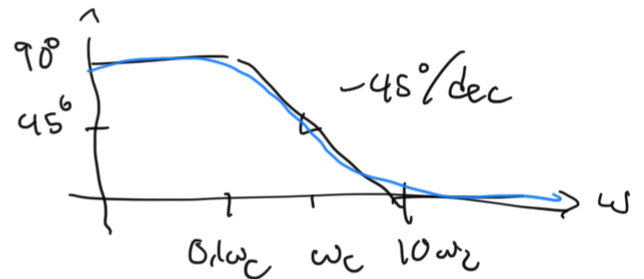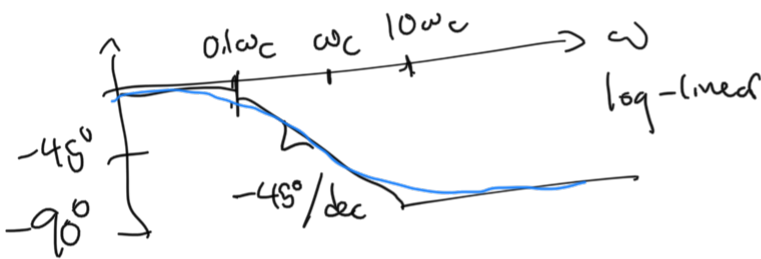

• Filters can be cascaded

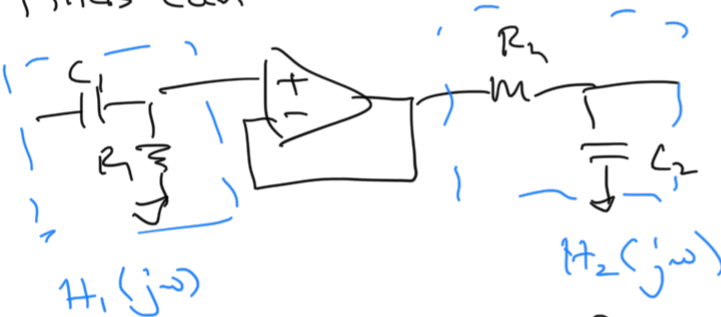

$$H_{\text{tot}}(j\omega) = H_1(j\omega) H_2(j\omega)$$

B/c of log-properties,

multiplication \longrightarrow add plots.



• Poles and Zeros


$$H(j\omega) = K \frac{(j\omega)^{N_{z0}} \left(1 + \frac{j\omega}{\omega_{z1}}\right) \left(1 + \frac{j\omega}{\omega_{z2}}\right) \dots}{(j\omega)^{N_{p0}} \left(1 + \frac{j\omega}{\omega_{p1}}\right) \left(1 + \frac{j\omega}{\omega_{p2}}\right) \dots}$$

zeros

poles

In the log-log magnitude plot,

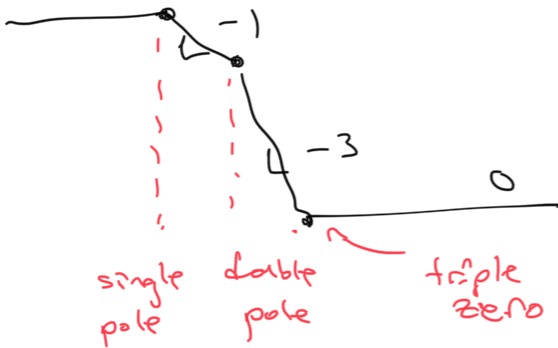- a) Each zero adds an additional slope of +1
- b) Each pole adds an additional slope of -1
- c) poles and zeros can cancel



VI. Resonance



Impedances of L and C cancel



$$j\omega C \cdot V$$

$$\Rightarrow \frac{1}{j\omega C} + j\omega L = 0$$
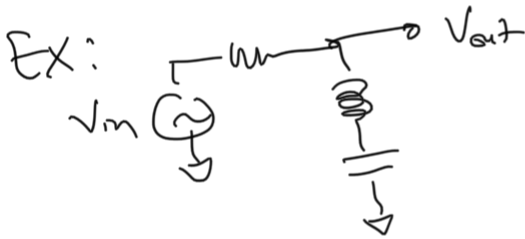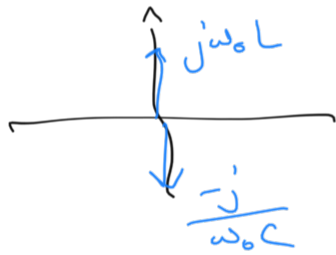
$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$




Antiresonant RLC Notch Filter

At $\omega = \omega_0$, looks like:




$$\Rightarrow V_{out} = 0$$

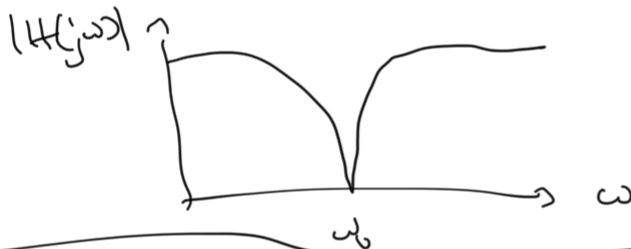

① Circuits Review


WS, Q7 (Passing a Clock)

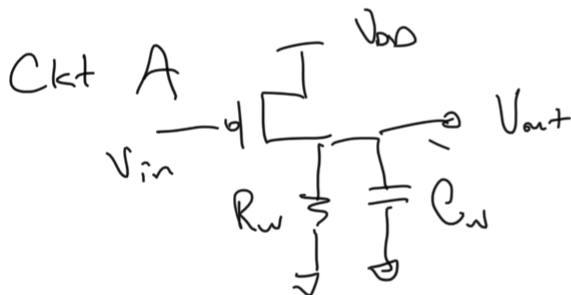


$$R_w = 500 \Omega$$

$$C_w = 3 \mu F$$

Ckt B

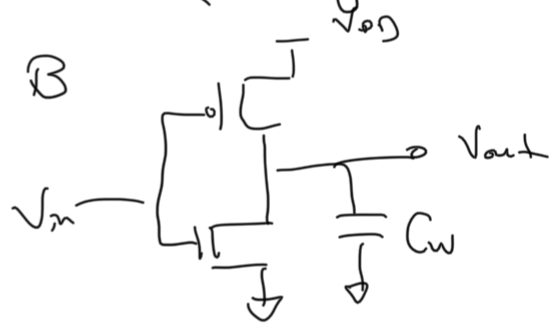


$$|V_{th}| = 0.7 \text{ V}$$

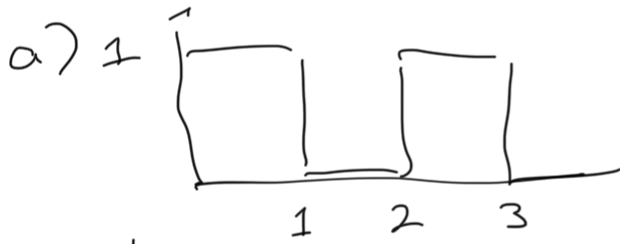


Ckt A: $R_p = 1 \text{ k}\Omega$

$$C_p = 5 \text{ nF}$$

$$V_{out}(0) = V_{DD}$$

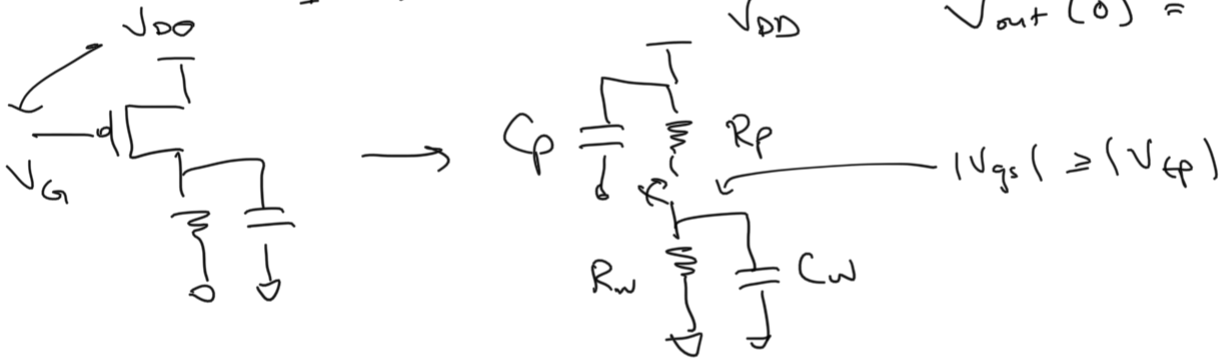

$t=0$: V_{in} switches to HIGH, PMOS off

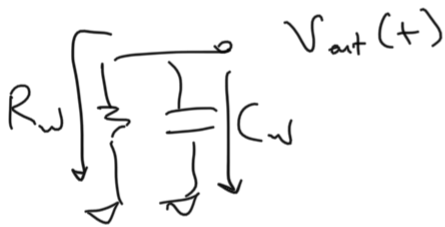

$$V_{out}(0) = V_{DD}$$

Expect: $V_{out}(t)$ \rightarrow discharging

$$V_{out}(t) = V_{DD} e^{-t/RC}$$


$T \in [0, 1)$

$$\frac{V_{out}}{R_w} + i_{C_w} = \frac{V_{out}}{R_w} + C_w \frac{dV_{out}}{dt} = 0$$


$$\frac{dV_{out}}{dt} = - \frac{1}{R_w C_w} V_{out}$$

$$V_{out}(t) = V_{out}(0) e^{-t/R_w C_w}$$

$$\tau_{A1} = R_w C_w = 500 \Omega \cdot 3 \mu F = 1.5 \text{ ms}$$



$$t \in [1, 2)$$

$$\tau_{A1} \ll 1 \text{ s}$$

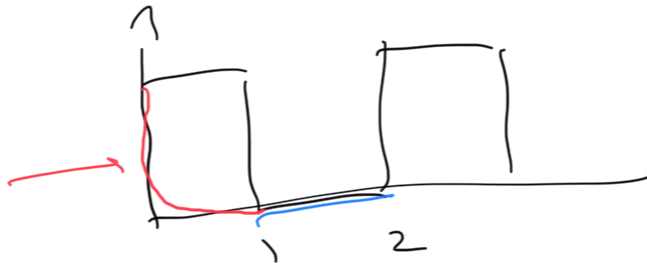

$$V_{out}(1) = 0$$

V_m low, PMOS ON

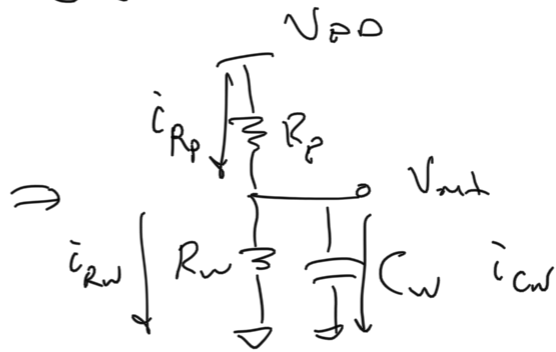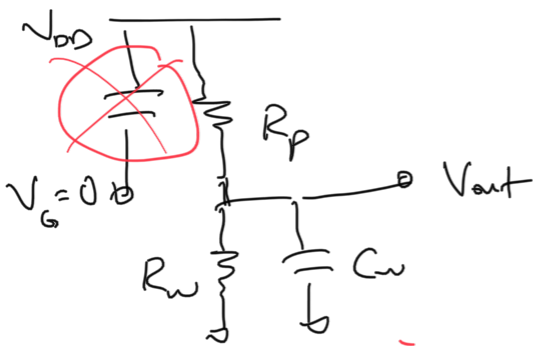

$$\frac{V_{DD} - V_{out}}{R_p} = \frac{V_{out}}{R_w} + C_w \frac{dV_{out}}{dt}$$

Expect: RC charging curve

$$\frac{dV_{out}}{dt} = \frac{V_{DD}}{R_p C_w} - \frac{V_{out}}{R_p C_w} - \frac{V_{out}}{R_w C_w}$$

$$= \frac{V_{DD}}{R_p C_w} - V_{out} \left(\frac{1}{R_p} + \frac{1}{R_w} \right) \frac{1}{C_w}$$

$$= \frac{V_{DD}}{R_p C_w} - V_{out} \left(\frac{R_p + R_w}{R_p R_w C_w} \right)$$

$$= - \left(\frac{R_p + R_w}{R_p R_w C_w} \right) \left[V_{out} - \frac{V_{DD}}{R_p C_w} \frac{R_p R_w C_w}{R_p + R_w} \right]$$

$$= - \left(\frac{R_p + R_w}{R_p R_w C_w} \right) \left[V_{out} - V_{DD} \frac{R_w}{R_p + R_w} \right]$$

$$\hat{V}_{out} = V_{out} - V_{DD} \frac{R_w}{R_p + R_w}$$

$$\frac{d\hat{V}_{out}}{dt} = \frac{dV_{out}}{dt}$$

$$\Rightarrow \frac{d\hat{V}_{out}}{dt} = - \left(\frac{R_p + R_w}{R_p R_w C_w} \right) \hat{V}_{out}$$

$$\hat{V}_{out}(t) = \hat{V}_{out}(1) e^{- (t-1) \left(\frac{R_p + R_w}{R_p R_w C_w} \right)}$$

$$V_{out} - () V_{DD} = \left[\cancel{V_{out}(1)} - () V_{DD} \right] e^{\frac{-(t-1)}{\tau}} \tau = (R_p || R_w) C_w$$


$$V_{out} = \frac{R_w}{R_p + R_w} V_{DD} \left(1 - e^{- (t-1) / \tau_{A2}} \right)$$

$$\text{where } \tau_{A2} = (R_p || R_w) C_w$$

$$\tau_{A2} = \left(\frac{1}{500} + \frac{1}{1000} \right)^{-1} 3 \mu\text{F}$$

$$= \frac{1}{3} \text{ k}\Omega \cdot 3 \mu\text{F} = 1 \text{ ms}$$

$$\tau_{A2} \ll 1 \text{ s},$$

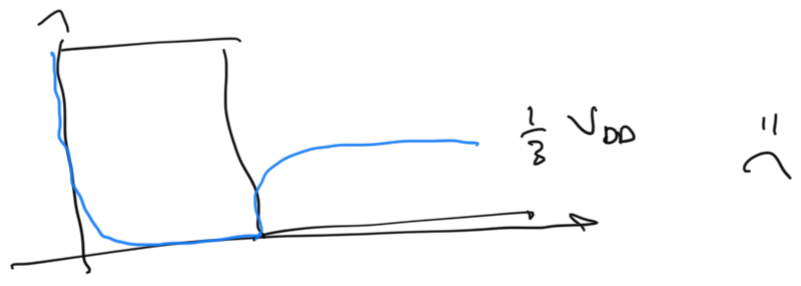


$$V_{out}(t) = \frac{R_{th}}{R_p + R_{th}} V_{DD} (1 - e^{-t/\tau})$$


$$= \frac{1}{3} V_{DD} (1 - e^{-t/\tau})$$

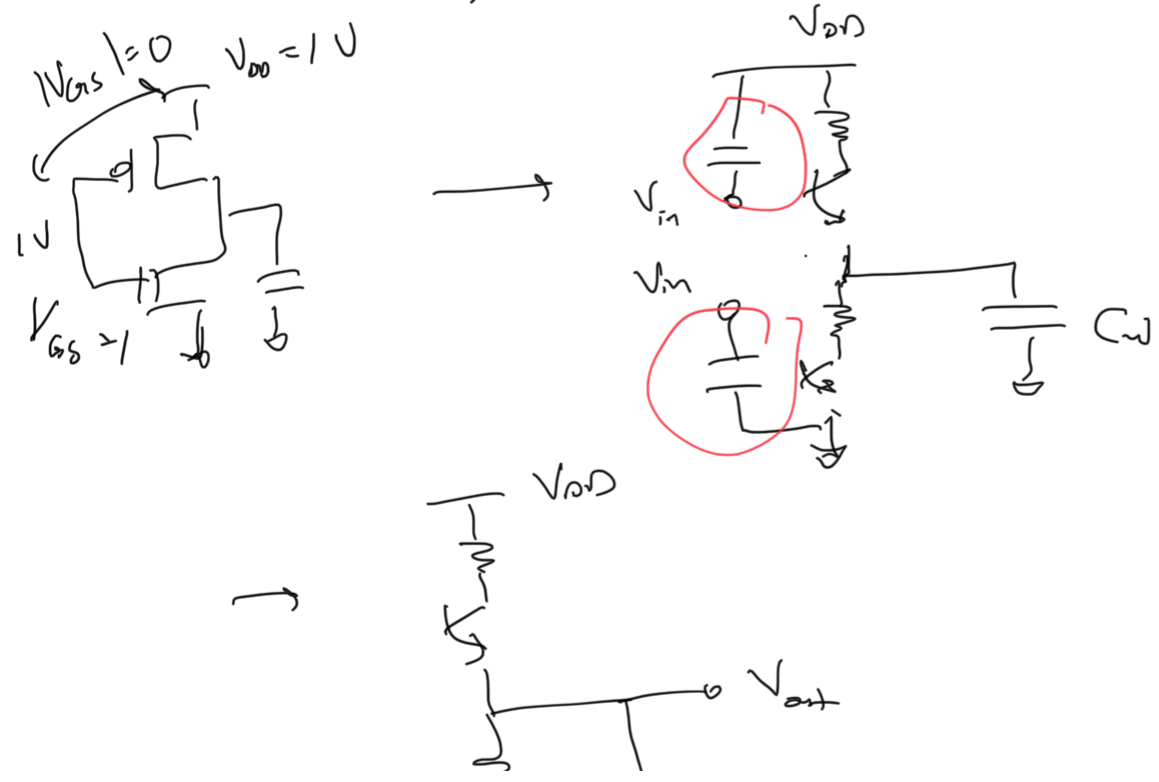b) CH B

$$R_p = 1 \text{ k}\Omega, C_p = 5 \mu\text{F}$$

$$R_n = 1 \text{ k}\Omega, C_n = 2 \mu\text{F}$$



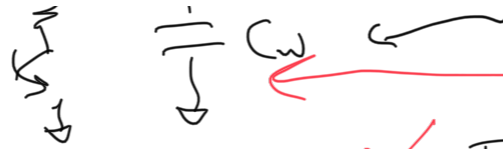


$t = 0 : V_{out}(0) = V_{DD}$


$V_m = \text{HIGH}$



NMOS on, PMOS off

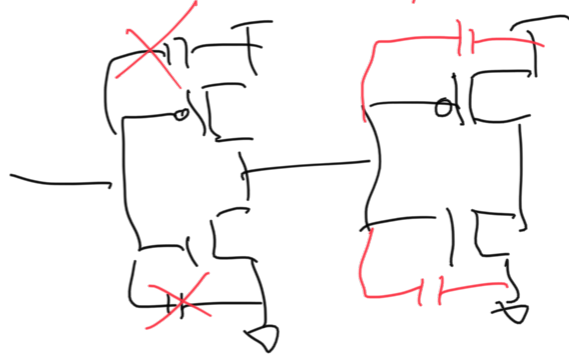


$t \in [0, 1)$

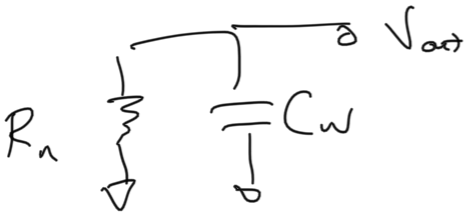

$\tau_{B1} = R_n C_w$

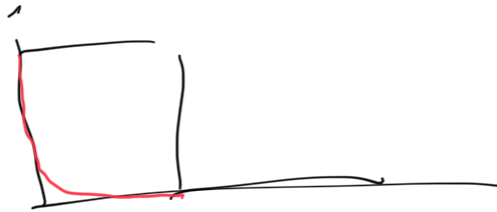$\Rightarrow \begin{cases} V_{out}(t) = V_{DD} e^{-t/R_n C_w} \\ \tau_{B1} = 1 \mu\Omega + 3 \mu F = 3 \text{ms} \end{cases}$




t

$V_{out}(1) = 0$

$t \in [1, 2)$


\Rightarrow PMOS on, NMOS off

$$V_m = LOW$$

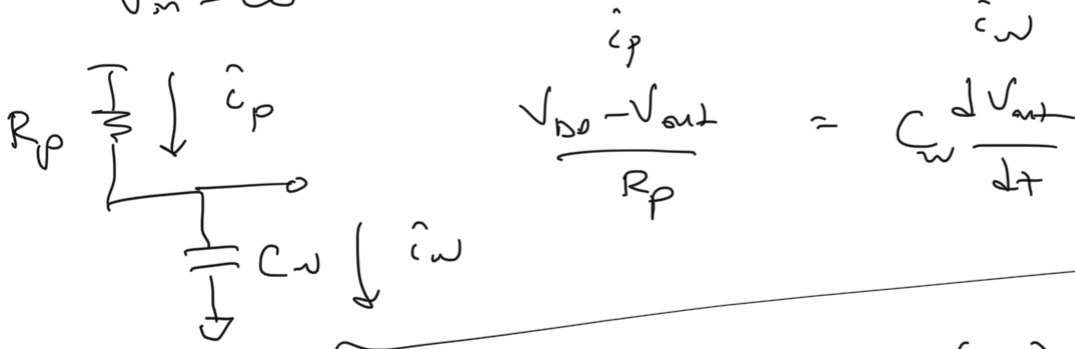

$$\frac{V_{DD} - V_{out}}{R_p} = C_w \frac{dV_{out}}{dt}$$

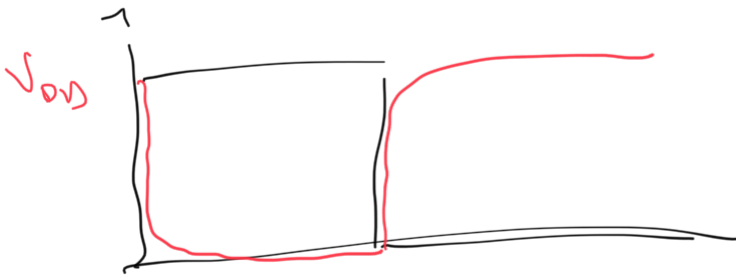
$$\Rightarrow \left[\begin{aligned} V_{out}(t) &= V_{DD} (1 - e^{-(t-1)/R_p C_w}) \\ \tau_{B2} &= R_p C_w = 3 \text{ ms} \end{aligned} \right]$$



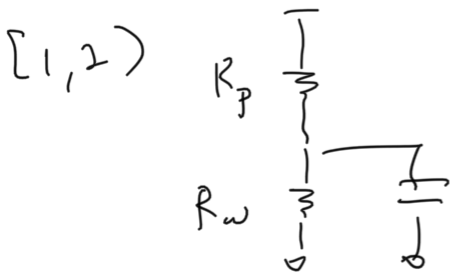c) Energy dissipation



$$\left[\begin{aligned} U &= \frac{1}{2} C_w V_{DD}^2 \\ &= 1.5 \times 10^{-6} V_{DD}^2 \end{aligned} \right]$$



$$U = \int P(t) dt = \int I(t) V_{DD} dt$$



charges super quickly:
approximate capacitor as
instantly



being charged ... 0

$$P = \frac{V_{DD}^2}{R_p + R_w}$$

$$U = \int_0^2 P dt = \frac{V_{DD}^2}{R_p + R_w} \times 1 \text{ s}$$

$$= 0.33 \times 10^{-3} V_{DD}^2$$

Model B:



$$U = \frac{1}{2} C_w V_{DD}^2 = 1.5 \times 10^{-6} V_{DD}^2$$

$$U = \frac{1}{2} C_w V_{DD}^2 = 1.5 \times 10^{-6} V_{DD}^2$$

Clearly, model A dissipates more energy

↓) Speed?

Total delay for ckt A: $\tau_{1A} + \tau_{2A} = 1.5 \text{ ns} + 1 \text{ ns}$

$$= \boxed{2.5 \text{ ns}}$$

" " ckt B: $\tau_{1B} + \tau_{2B} = 3 \text{ ns} + 3 \text{ ns}$

$$= \boxed{6 \text{ ns}}$$

Ckt A is faster,
but at the cost of more energy dissipation

2.